

## Homework Assignment III

**Reading Assignment:** Lecture Notes; Kerns-Irwin Chapter 3.

1. Consider a simple RC circuit with a DC voltage source  $V_S$  sketched below. At some time in the distant past, the DC voltage source was connected to the circuit to charge up the capacitor  $C$ . You can assume that  $C$  has been fully charged prior to  $t = 0$ .

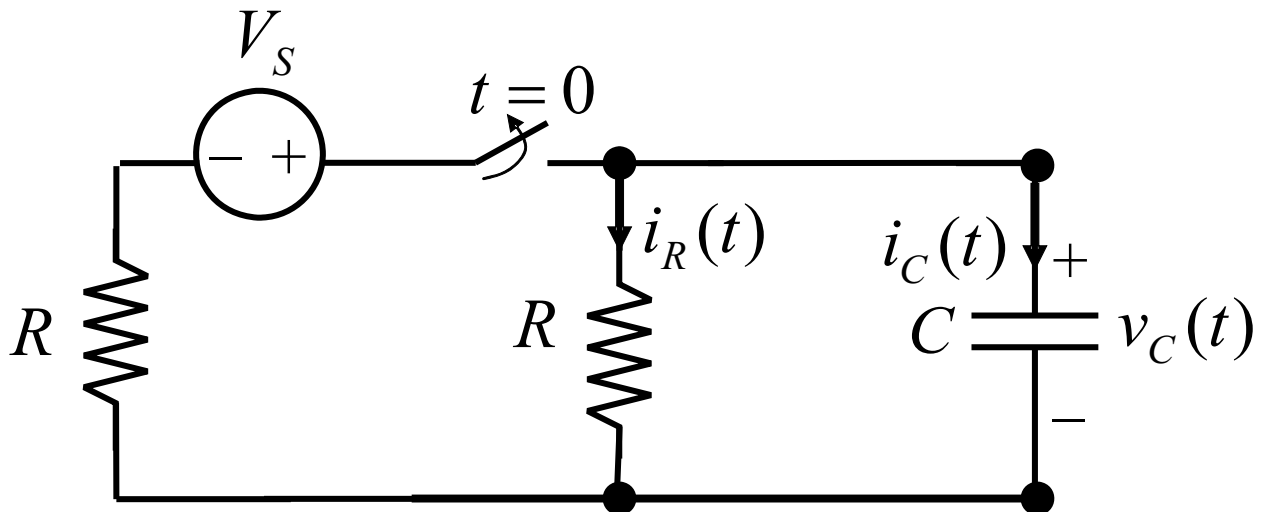


Figure 1: RC Circuit with a DC Voltage Source.

- (a) Find the voltage that the capacitor is charged up to right before  $t = 0$ . *Hint: In DC steady state, the capacitor behaves as an open circuit.*
- (b) The switch opens at  $t = 0$ . Find the differential equation describing the behavior of  $v_C(t)$  after the switch opens ( $t > 0$ ).
- (c) Find the expression for the voltage across the capacitor  $v_C(t)$  for  $t > 0$ . Sketch it as a function of time.
- (d) Find and sketch the current  $i_R(t)$  through the middle resistor  $R$  after the switch opens.
- (e) Suppose that the switch will then be closed at a distant time  $t = T \gg RC$  ( $T$  is much larger than  $RC$ ) in the future. Re-sketch the voltage across the capacitor  $v_C(t)$  for  $t > 0$  taking into account this switch-closing situation. You do not have to find the exact expression for  $v_C(t)$ .

2. Consider an RC circuit with a DC current source  $I_S$  sketched below. At some time in the distant past, the DC current source was connected to the circuit to charge up the capacitor  $C$  (the switch stays open). You can assume that  $C$  has been fully charged prior to  $t = 0$ .

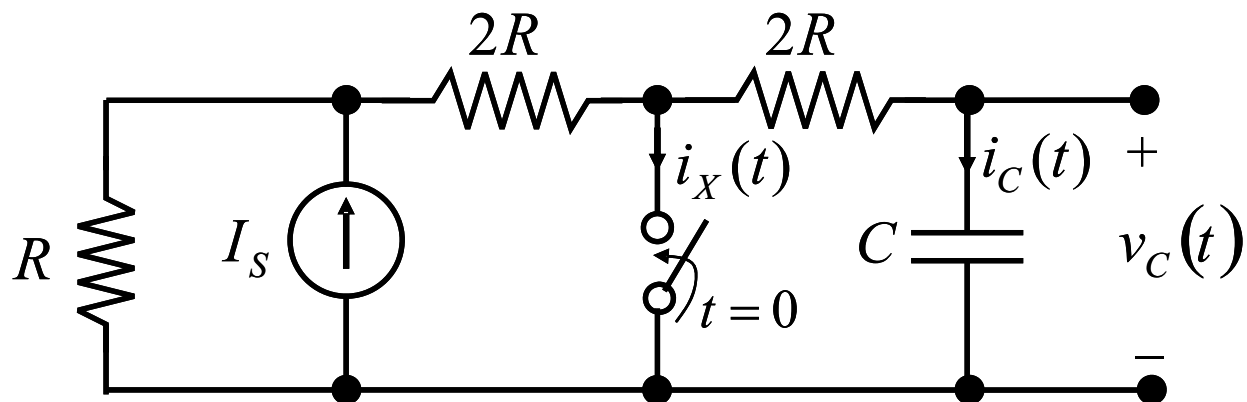


Figure 2: RC Circuit with a DC Current Source.

- The switch closes at  $t = 0$ . Find the differential equation describing the behavior of  $v_C(t)$  after the switch closes ( $t > 0$ ).
- Given that  $R = 5K\Omega$ ,  $C = 100\mu F$ , and  $I_S = 2mA$ , find the voltage that the capacitor is charged up to right before  $t = 0$ .
- Find the expression for the voltage across the capacitor  $v_C(t)$  for  $t \geq 0$  by solving the differential equation in Part (a) using the initial condition in Part (b). Sketch  $v_C(t)$  as a function of time.
- Find and sketch  $i_C(t)$  for  $t \geq 0$ .
- Find the current  $i_X$  through the switch branch a long time after the switch closes.

Due date: **Friday September 30th** in class