

## Homework Assignment II

**Reading Assignment:** Lecture Notes; Kerns-Irwin Chapter 3.

1. Consider the resistive circuit in a diamond topology on the left of the figure below. This is commonly known as the *Wheatstone Bridge*, often used in electrical measurement applications. Note that this circuit can be redrawn as shown on the right side.

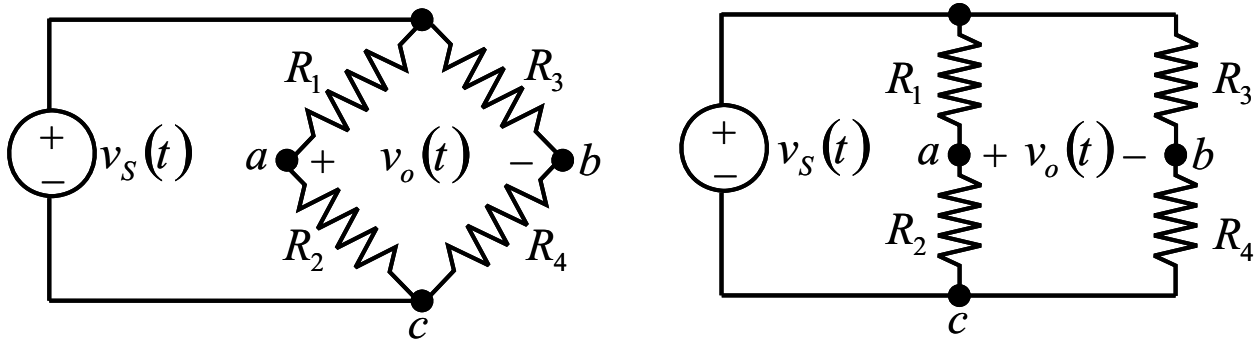


Figure 1: The Wheatstone Bridge.

- (a) Find  $v_{ac}(t)$  – the voltage across the resistor  $R_2$  – and  $v_{bc}(t)$  – the voltage across the resistor  $R_4$  – as a function of the source voltage  $v_S(t)$ .
- (b) Find  $v_o(t)$  – the voltage across nodes  $a$  and  $b$  – as a function of the source voltage  $v_S(t)$  given that  $R_1 = R_4$  and  $R_2 = R_3 = 2R_1$ . *Hint:*  $v_{ab}(t) = v_{ac}(t) - v_{bc}(t)$ .
- (c) If the source voltage is  $v_S(t) = 9 \cos(4\pi t)$ , find the period, frequency, average voltage  $V_{AVE}$ , and root-mean-squared voltage  $V_{RMS}$  for  $v_o(t)$ .
- (d) Sketch the instantaneous power  $p_S(t)$  generated by the voltage source given the same set-up as in Part (b) and (c).
- (e) If the stock room only carries  $1\Omega$  resistors, design and sketch your resulting Wheatstone Bridge where  $v_o(t)$  is always precisely  $\frac{1}{6}v_S(t)$ .
- (f) Suppose that the source voltage is  $v_S(t) = 9 \cos(4\pi t)$  and  $R_1 = 1\Omega$ ,  $R_2 = 2\Omega$ ,  $R_3 = 3\Omega$ ,  $R_4 = 4\Omega$ . Find the Thevenin equivalent circuit looking into the 2 terminals  $a$  and  $b$ .
- (g) With the same set-up as in Part (f), find the Norton equivalent circuit looking into the 2 terminals  $a$  and  $b$ .

2. The circuits below models the voltage produced by the generator of a power plant and  $R_S$  models the resistive losses in the generator, wire, and transformers. Resistances  $R_1$ ,  $R_2$ , and  $R_3$  represent the various loads connected by a customer. Assume that  $R_1 = R_2 = R_3 = R_S = R$ .

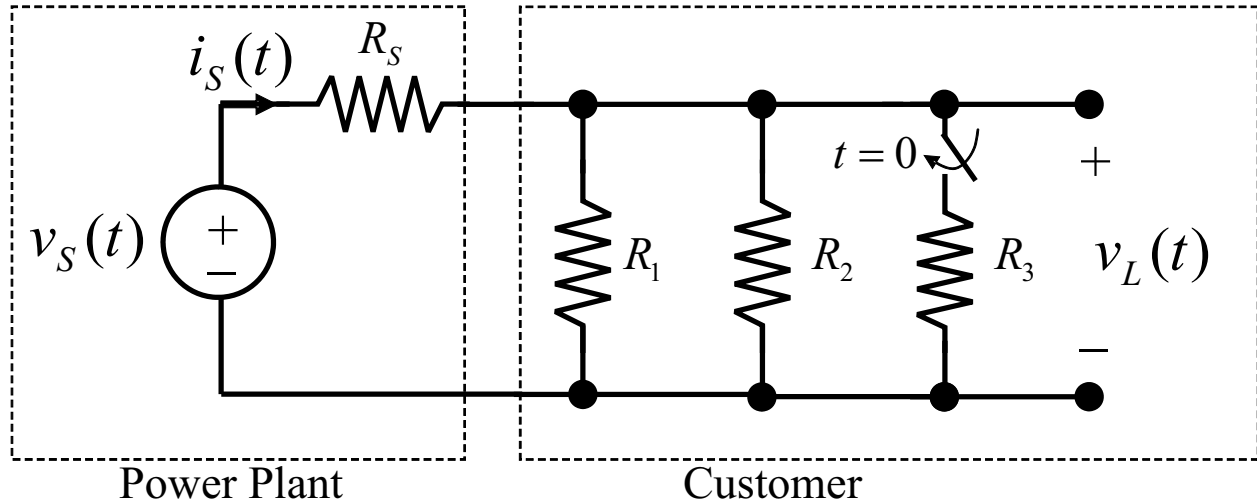


Figure 2: An electrical network model with power plant and consumers.

- Find the load voltage  $v_L(t)$  as a function of the source voltage  $v_S(t)$  for  $t < 0$  (before the customer closes the switch and connects the third load).
- Find the load voltage  $v_L(t)$  as a function of the source voltage  $v_S(t)$  for  $t > 0$  (after the customer closes the switch and connects the third load).
- Sketch the load voltage  $v_L(t)$  and the source current  $i_S(t)$  as functions of time assuming that  $v_S(t)$  is a DC source with peak value of  $150V$ .
- Sketch the source current  $i_S(t)$  as a function of time assuming that  $v_S(t)$  is a  $60Hz$  AC source with RMS value of  $170V$ .
- For the AC source above, how much energy does the voltage source at the power plant produce over one source period (cycle) before and after the switch is closed?
- Bonus:** What is the Thevenin and Norton equivalence (from the 2 right-most terminals) of this circuit if there are  $N$  connected customers in parallel?

Due date: **September 21** in class